

# Practice Problems - Chapter 33


## Alternating Current Circuits

### Multiple Choice


4. A high-voltage powerline operates at 500 000 V-rms and carries an rms current of 500 A. If the resistance of the cable is  $0.050\Omega/\text{km}$ , what is the resistive power loss in 200 km of the powerline?
- 250 kW
  - 500 kW
  - 1 Megawatt
  - 2.5 Megawatts
  - 250 Megawatts
12. A  $10\text{-}\mu\text{F}$  capacitor is plugged into a 110 V-rms 60-Hz voltage source, with an ammeter in series. What is the rms value of the current through the capacitor?
- 0.202 A (rms)
  - 0.415 A (rms)
  - 0.626 A (rms)
  - 0.838 A (rms)
  - 0.066 A (rms)
13. A 0.5-H inductor is connected into a 110 V-rms 60-Hz voltage source, with an ammeter in series. What is the rms value of the current through the inductor?
- 0.189 A (rms)
  - 0.292 A (rms)
  - 0.584 A (rms)
  - 1.19 A (rms)
  - 0.093 A (rms)
15. The inductance of a tuning circuit of an AM radio is 4 mH. Find the capacitance of the circuit required for reception at 1200 kHz.
- 2.1 pF
  - 4.4 pF
  - 21.2 pF
  - 43.4 pF
  - 27.6 pF
18. If an  $R = 1\text{-k}\Omega$  resistor, a  $C = 1\text{-}\mu\text{F}$  capacitor, and an  $L = 0.2\text{-H}$  inductor are connected in series with a  $V = 150 \sin(377t)$  volts source, what is the maximum current delivered by the source?
- 0.007 A
  - 27 mA
  - 54 mA
  - 0.308 A
  - 0.34 A

20. An  $RLC$  series circuit has  $R = 100$  ohms,  $C = 25 \mu\text{F}$ , and  $L = 0.16$  H. For what angular frequency of an ac voltage is the current flow maximum?
- 251 rad/s
  - 500 rad/s
  - 757 rad/s
  - 884 rad/s
  - 79.6 rad/s

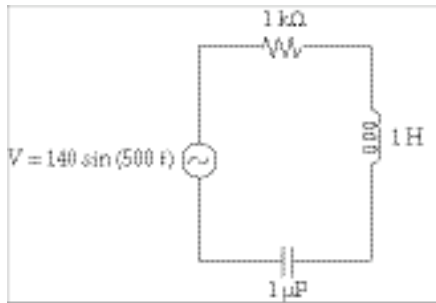22. Determine the impedance for the circuit.



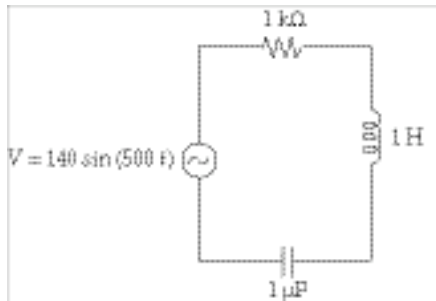
- 600  $\Omega$
  - 1200  $\Omega$
  - 1800  $\Omega$
  - 2300  $\Omega$
  - 1100  $\Omega$
23. Determine the rms current for the circuit.




- 55 mA
  - 77 mA
  - 99 mA
  - 0.190 A
  - 61 mA
30. What is the average power dissipation in an  $RLC$  series circuit with  $R = 10\Omega$ ,  $L = 0.1$  H,  $C = 10 \mu\text{F}$  when driven at resonance by a 100 V-rms source?
- 100 W
  - 500 W
  - 1000 W
  - 2 kW
  - 700 W

32. A transformer is to be designed to increase the 30 kV-rms output of a generator to the transmission-line voltage of 345 kV-rms. If the primary winding has 80 turns, how many turns must the secondary have?
- 6
  - 70
  - 920
  - 9200
  - 12
33. The primary winding of an electric train transformer has 400 turns and the secondary has 50. If the input voltage is 120V(rms) what is the output voltage?
- 15 V (rms)
  - 30 V (rms)
  - 60 V (rms)
  - 2.4 V (rms)
  - 960 V (rms)

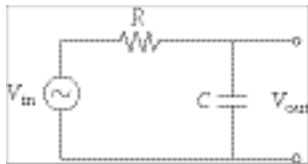37. Calculate  $V_{\text{out}}/V_{\text{in}}$  for the circuit if  $R = 2 \text{ k}\Omega$ ,  $C = 0.02 \mu\text{F}$  and  $V = 140\text{V} \sin(50\,000t)$




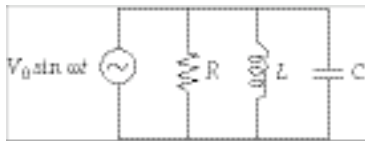- 0.02
  - 0.45
  - 0.80
  - 0.98
  - 2.23
38. The impedance of the parallel  $RLC$  circuit shown is given by




- $\frac{1}{R} + \frac{1}{\omega L} + \omega C$
- $\left[ \frac{1}{R^2} + \left( \omega C - \frac{1}{\omega L} \right)^2 \right]^{-1/2}$
- $\frac{1}{R} + \left( \frac{1}{\omega L} - \frac{1}{\omega C} \right)$
- $\sqrt{R^2 + \left( \omega L - \frac{1}{\omega C} \right)^2}$
- $\sqrt{\frac{1}{R^2} + \left[ \omega C - \frac{1}{\omega L} \right]^2}$

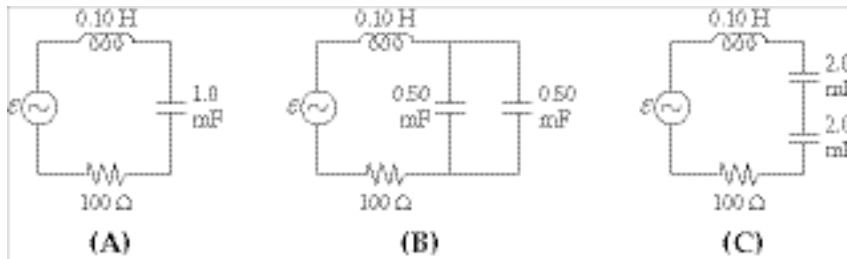46. Whenever the alternating current frequency in a series  $RLC$  circuit is halved,
- the inductive reactance is doubled and the capacitive reactance is halved.
  - the inductive reactance is doubled and the capacitive reactance is doubled.
  - the inductive reactance is halved and the capacitive reactance is halved.
  - the inductive reactance is halved and the capacitive reactance is doubled.
  - the reactance of the circuit remains the same.
47. The average power input to a series alternating current circuit is minimum when
- there are only a resistor and capacitor in the circuit.
  - there are only a resistor and inductor in the circuit.
  - there is only a resistor in the circuit.
  - $X_L = X_C$  and the circuit contains a resistor, an inductor and a capacitor.
  - there is only a capacitor in the circuit.
48. All three circuits shown below have  $R = 100 \Omega$ ,  $L = 0.1 \text{ H}$  and emf  $\mathcal{E} = (5.0 \text{ V}) \sin(377 t)$ . Which statement regarding the angular resonance frequencies  $\omega_A$ ,  $\omega_B$  and  $\omega_C$  is correct?



- $\omega_C > \omega_A = \omega_B$
  - $\omega_C < \omega_A = \omega_B$
  - $\omega_A = \omega_B = \omega_C$
  - $\omega_B < \omega_A = \omega_C$
  - $\omega_B > \omega_A = \omega_C$
56. A  $10\text{-}\mu\text{F}$  capacitor in an  $LC$  circuit made entirely of superconducting materials ( $R = 0 \Omega$ ) is charged to  $100 \mu\text{C}$ . Then a superconducting switch is closed. At  $t = 0 \text{ s}$ , plate 1 is positively charged and plate 2 is negatively charged. At a later time,  $V_{ab} = +10 \text{ V}$ . At that time,  $V_{dc}$  is

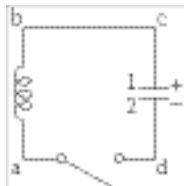

- $0 \text{ V}$ .
- $3.54 \text{ V}$ .
- $5.0 \text{ V}$ .
- $7.07 \text{ V}$ .
- $10 \text{ V}$ .

## Open-Ended Problems

57. Suppose the circuit parameters in a series  $RLC$  circuit are:  $L = 1.0 \mu\text{H}$ ,  $C = 10.0 \text{ nF}$ ,  $R = 100\Omega$ , and the source voltage is  $220 \text{ V}$ . Determine the resonant frequency of the circuit and the amplitude of the current at resonance.
58. A  $10\text{-}\Omega$  resistor,  $10\text{-mH}$  inductor, and  $10\text{-}\mu\text{F}$  capacitor are connected in series with a  $10\text{-kHz}$  voltage source. The rms current through the circuit is  $0.20 \text{ A}$ . Find the rms voltage drop across each of the 3 elements.
59. An ac power generator produces  $50 \text{ A}$  (rms) at  $3600 \text{ V}$ . The voltage is stepped up to  $100\,000 \text{ V}$  by an ideal transformer and the energy is transmitted through a long distance power line which has a resistance of  $100 \text{ ohms}$ . What percentage of the power delivered by the generator is dissipated as heat in the long-distance power line?

## Chapter 33

### Alternating Current Circuits

- |     |   |     |   |
|-----|---|-----|---|
| 1.  | c | 29. | b |
| 2.  | a | 30. | c |
| 3.  | d | 31. | a |
| 4.  | d | 32. | c |
| 5.  | d | 33. | a |
| 6.  | a | 34. | b |
| 7.  | a | 35. | d |
| 8.  | b | 36. | d |
| 9.  | a | 37. | b |
| 10. | d | 38. | b |
| 11. | d | 39. | b |
| 12. | b | 40. | a |
| 13. | c | 41. | e |
| 14. | d | 42. | c |
| 15. | b | 43. | d |
| 16. | b | 44. | a |
| 17. | c | 45. | d |
| 18. | c | 46. | d |
| 19. | d | 47. | e |
| 20. | b | 48. | c |
| 21. | a | 49. | c |
| 22. | c | 50. | a |
| 23. | a | 51. | d |
| 24. | a | 52. | c |
| 25. | a | 53. | b |
| 26. | b | 54. | d |
| 27. | c | 55. | d |
| 28. | b | 56. | e |

- 57. 1.59 MHz, 2.2 A
- 58. 2.0 V, 125.6 V, 0.318 V
- 59. 0.18%